

$$V_{\max} = I_{\max} R$$

$$= 10 \times 10 = 100 \text{ V}$$

$$\omega = 2\pi f = 2\pi(60)$$

$$= 120\pi \text{ rad/s}$$

$$\Delta v = 100 \sin 120\pi t$$

$$= 100 \sin(120\pi(0.3))$$

$$= 0$$

$$\Delta v = V_{\max} \sin \omega t \quad : Q_4$$

$$90 = 360 \sin \omega t$$

$$0.25 = \sin \frac{\omega}{200}$$

$$0.25 = \frac{\omega}{200}$$

$$\omega = 50 \text{ rad/s}$$

$$\omega = 2\pi f$$

$$50 = 2\pi f$$

$$f = 7.96 \text{ Hz}$$

$$I_{\max} = \frac{V_{\max}}{R} = \frac{360}{50}$$

$$= 7.2 \text{ A}$$

$$I_{\text{rms}} = 0.71 \times 7.2$$

$$= 5.11 \text{ A}$$

$$- I_{\text{rms}} = 0.71 I_{\max}$$

$$= 0.71 \times 2$$

$$= 1.42 \text{ A}$$

$$- T = 8 \times 10^{-3} \text{ s}$$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{8 \times 10^{-3}} = \frac{\pi}{4 \times 10^{-3}} \text{ rad/s}$$

$$i = I_{\max} \sin \omega t$$

$$i = 2 \sin \frac{\pi}{4 \times 10^{-3}} t$$

$$- I_{\max} = \frac{V_{\max}}{R} \quad : Q_2$$

$$= \frac{50}{20} = 2.5 \text{ A}$$

$$I_{\text{rms}} = 0.71 I_{\max}$$

$$= 0.71 \times 2.5$$

$$= 1.775 \text{ A}$$

$$- \omega = 2\pi f = 2\pi \times 50$$

$$= 60\pi \text{ rad/s}$$

$$i = I_{\max} \sin \omega t$$

$$i = 2.5 \sin 60\pi t$$

- يَبْنَ لِعَبَّة لِعَبَّر لِنَا كَابَّ

$$I_{\text{rms}} = 0.71 I_{\max} \quad : Q_3$$

$$7.1 = 0.71 I_{\max}$$

$$I_{\max} = 10 \text{ A}$$

$$I_{\max} = \frac{V_{\max}}{R} = \frac{220}{11} \quad \therefore Q_5$$
$$= 20 \text{ A}$$

$$I_{\text{rms}} = 0.71 I_{\max}$$
$$= 0.71 \times 20$$
$$= 14.2 \text{ A}$$

$I_{\text{rms}}$  قراءة الأمبير  $\therefore Q_6$

$V_{\text{rms}}$  قراءة الفولت  $\therefore Q_6$

$$V_{\text{rms}} = 0.71 V_{\max}$$
$$= 0.71 \times 100$$
$$= 71 \text{ V} \quad \text{قراءة الفولت}$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{71}{240}$$
$$= 0.296 \text{ A}$$

قراءة الأمبير

$$V_{\text{rms}} = 0.71 V_{\max} \quad \therefore Q_7$$
$$= 0.71 \times 324$$
$$= 230 \text{ V}$$